




# Applications of DEs: Simple LRC circuits

Prof. Joyner<sup>1</sup>

An LRC circuit is a closed loop containing an inductor of  $L$  henries, a resistor of  $R$  ohms, a capacitor of  $C$  farads, and an EMF (electro-motive force), or battery, of  $E(t)$  volts, all connected in series.

They arise in several engineering applications. For example, AM/FM radios with analog tuners typically use an LRC circuit to tune a radio frequency. Most commonly a variable capacitor is attached to the tuning knob, which allows you to change the value of  $C$  in the circuit and tune to stations on different frequencies [R].

We use the following “dictionary” to translate between the diagram and the DEs.
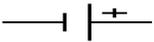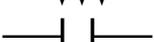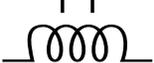
| EE object | term in DE<br>(the voltage drop) | units         | symbol  |
|-----------|----------------------------------|---------------|---|
| charge    | $q = \int i(t) dt$               | coulombs      |   |
| current   | $i = q'$                         | amps          |   |
| emf       | $e = e(t)$                       | volts $V$     |  |
| resistor  | $Rq' = Ri$                       | ohms $\Omega$ |  |
| capacitor | $C^{-1}q$                        | farads        |  |
| inductor  | $Lq'' = Li'$                     | henries       |  |

*Kirchoff's First Law:* The algebraic sum of the currents travelling into any node is zero.

*Kirchoff's Second Law:* The algebraic sum of the voltage drops around any closed loop is zero.

---

<sup>1</sup>These notes licensed under Attribution-ShareAlike Creative Commons license, <http://creativecommons.org/about/licenses/meet-the-licenses>. The diagrams were created using Dia <http://www.gnome.org/projects/dia/> and GIMP <http://www.gimp.org/> by the author. Originally written 9-21-2007. Last updated 2008-11-28.

Generally, the charge at time  $t$  on the capacitor,  $q(t)$ , satisfies the DE

$$Lq'' + Rq' + \frac{1}{C}q = e(t). \quad (1)$$

When there is no EMF, sometimes the following terminology is used. If  $R > 2\sqrt{L/C}$  (“ $R$  is large”) then the circuit is called **overdamped**. If  $R = 2\sqrt{L/C}$  (“ $R$  is large”) then the circuit is called **critically-damped**. If  $0 \leq R < 2\sqrt{L/C}$  (“ $R$  is large”) then the circuit is called **underdamped**.

**Example 1:** Consider the simple LC circuit given by the diagram in Figure 1.

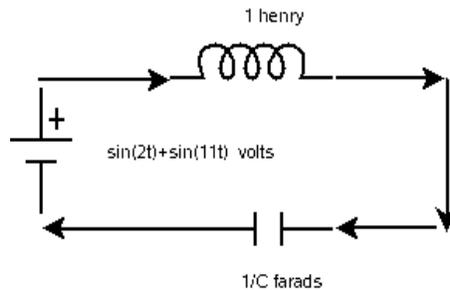


Figure 1: A simple LC circuit.

This is a simple model illustrating the idea of a radio tuner (the variable capacitor) which can tune into only two stations, “channel 2” and “channel 11”.

According to Kirchoff’s  $2^{nd}$  Law and the above “dictionary”, this circuit corresponds to the DE

$$q'' + \frac{1}{C}q = \sin(2t) + \sin(11t).$$

The homogeneous part of the solution is

$$q_h(t) = c_1 \cos(t/\sqrt{C}) + c_2 \sin(t/\sqrt{C}).$$

If  $C \neq 1/4$  and  $C \neq 1/121$  then

$$q_p(t) = \frac{1}{C^{-1} - 4} \sin(2t) + \frac{1}{C^{-1} - 121} \sin(11t).$$

When  $C = 1/4$  and the initial charge and current are both zero, the solution is

$$q(t) = -\frac{1}{117} \sin(11t) + \frac{161}{936} \sin(2t) - \frac{1}{4}t \cos(2t).$$

```

SAGE

sage: t = var("t")
sage: q = function("q",t)
sage: L,R,C = var("L,R,C")
sage: e = lambda t: sin(2*t)+sin(11*t)
sage: de = lambda y: L*difff(y,t,t) + R*difff(y,t) + (1/C)*y-e(t)
sage: L,R,C=1,0,1/4
sage: de(q(t))
diff(q(t), t, 2) - sin(11*t) - sin(2*t) + 4*q(t)
sage: desolve(de(q(t)),[q,t])
(-4*sin(11*t) - 117*t*cos(2*t))/468 + k1*sin(2*t) + k2*cos(2*t)
sage: desolve_laplace(de(q(t)),["t","q"],[0,0,0])
'-sin(11*t)/117+161*sin(2*t)/936-t*cos(2*t)/4'
sage: soln = lambda t: -sin(11*t)/117+161*sin(2*t)/936-t*cos(2*t)/4
sage: P = plot(soln,0,10)
sage: show(P)

```

This is displayed in Figure 2.

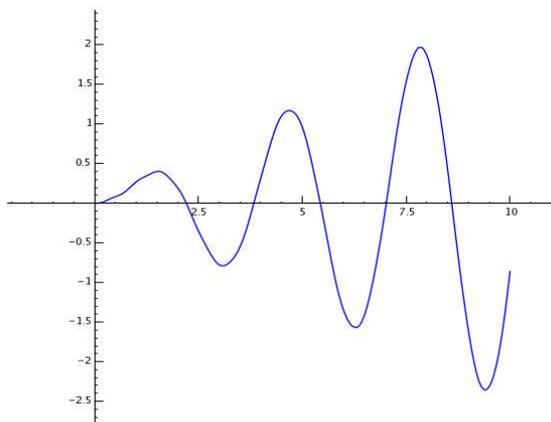


Figure 2: A LC circuit, with resonance.

You can see how the frequency  $\omega = 2$  dominates the other terms.

When  $0 < R < 2\sqrt{L/C}$  the homogeneous form of the charge in (1) has the form

$$q_h(t) = c_1 e^{\alpha t} \cos(\beta t) + c_2 e^{\alpha t} \sin(\beta t),$$

where  $\alpha = -R/2L < 0$  and  $\beta = \sqrt{4L/C - R^2}/(2L)$ . This is sometimes called the **transient part** of the solution. The remaining terms in the charge are called the **steady state terms**.

**Example:** An LRC circuit has a 1 henry inductor, a 2 ohm resistor, 1/5 farad capacitor, and an EMF of  $50 \cos(t)$ . If the initial charge and current is 0, since the charge at time  $t$ .

The IVP describing the charge  $q(t)$  is

$$q'' + 2q' + 5q = 50 \cos(t), \quad q(0) = q'(0) = 0.$$

The homogeneous part of the solution is

$$q_h(t) = c_1 e^{-t} \cos(2t) + c_2 e^{-t} \sin(2t).$$

The general form of the particular solution using the method of undetermined coefficients is

$$q_p(t) = A_1 \cos(t) + A_2 \sin(t).$$

Solving for  $A_1$  and  $A_2$  gives

$$q_p(t) = -10e^{-t} \cos(2t) - \frac{15}{2}e^{-t} \sin(2t).$$

SAGE

```
sage: t = var("t")
sage: q = function("q",t)
sage: L,R,C = var("L,R,C")
sage: E = lambda t: 50*cos(t)
sage: de = lambda y: L*diff(y,t,t) + R*diff(y,t) + (1/C)*y-E(t)
sage: L,R,C = 1,2,1/5
sage: de(q(t))
diff(q(t), t, 2) + 2*diff(q(t), t, 1) + 5*q(t) - 50*cos(t)
sage: desolve_laplace(de(q(t)),["t","q"],[0,0,0])
```

```
'%e^{-t}*(-15*sin(2*t)/2-10*cos(2*t))+5*sin(t)+10*cos(t)'
sage: soln = lambda t:\
    e^{(-t)*(-15*sin(2*t)/2-10*cos(2*t))+5*sin(t)+10*cos(t)}
sage: P = plot(soln,0,10)
sage: show(P)
sage: P = plot(soln,0,20)
sage: show(P)
sage: soln_ss = lambda t: 5*sin(t)+10*cos(t)
sage: P_ss = plot(soln_ss,0,10)
sage: soln_tr = lambda t: e^{(-t)*(-15*sin(2*t)/2-10*cos(2*t))}
sage: P_tr = plot(soln_tr,0,10,linestyle="--")
sage: show(P+P_tr)
```

This plot (the solution superimposed with the transient part of the solution) is displayed in Figure 3.

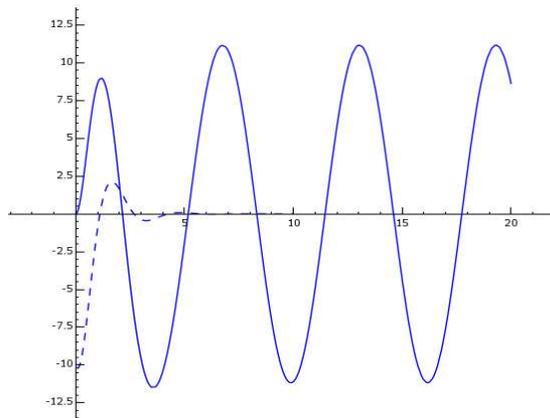


Figure 3: A LRC circuit, with damping, and the transient part (dashed) of the solution.

**Exercise:** Use SAGE to solve

$$q'' + \frac{1}{C}q = \sin(2t) + \sin(11t), \quad q(0) = q'(0) = 0,$$

in the case  $C = 1/121$ .

## References

- [KL] Wikipedia entry for Kirchhoff's laws:  
[http://en.wikipedia.org/wiki/Kirchhoffs\\_circuit\\_laws](http://en.wikipedia.org/wiki/Kirchhoffs_circuit_laws)
- [K] Wikipedia entry for Kirchhoff: [http://en.wikipedia.org/wiki/Gustav\\_Kirchhoff](http://en.wikipedia.org/wiki/Gustav_Kirchhoff)
- [N] Wikipedia entry for Electrical Networks:  
[http://en.wikipedia.org/wiki/Electrical\\_network](http://en.wikipedia.org/wiki/Electrical_network)
- [R] General wikipedia introduction to LRC circuits:  
[http://en.wikipedia.org/wiki/RLC\\_circuit](http://en.wikipedia.org/wiki/RLC_circuit)